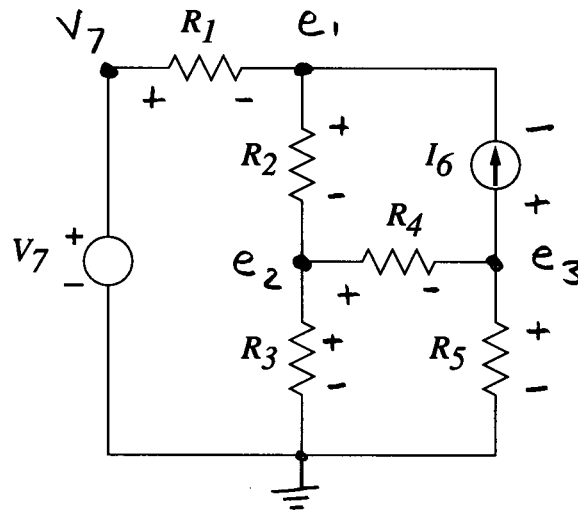


1. The first steps are to label the node potentials (to allow solution by the node method) and to label each element with +/- signs (so we can talk about branch currents, voltages).



Next, we write KCL at each node with unknown potential. This can be done "by inspection," as in class:

$$e_1: \left(\frac{1}{R_1} + \frac{1}{R_2} \right) e_1 - \frac{1}{R_2} e_2 = \frac{1}{R_1} V_7 + I_6$$

$$e_2: -\frac{1}{R_2} e_1 + \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) e_2 - \frac{1}{R_4} e_3 = 0$$

$$e_3: -\frac{1}{R_4} e_2 + \left(\frac{1}{R_4} + \frac{1}{R_5} \right) e_3 = -I_6$$

Plugging in values, we have that:

$$\frac{5}{6} e_1 - \frac{1}{2} e_2 = 6$$

$$-\frac{1}{2} e_1 + \frac{7}{6} e_2 - \frac{1}{3} e_3 = 0$$

$$-\frac{1}{3} e_2 + \frac{4}{3} e_3 = -5$$

(I've dropped units here.) We can solve by Cramer's rule, Gaussian elimination, calculator, etc. The result is

$e_1 = 9 \text{ V}$
$e_2 = 3 \text{ V}$
$e_3 = -3 \text{ V}$

The branch voltages are just the difference in node potentials across each element:

$v_1 = -6 \text{ V}$
$v_2 = 6 \text{ V}$
$v_3 = 3 \text{ V}$
$v_4 = 6 \text{ V}$
$v_5 = -3 \text{ V}$
$v_6 = -12 \text{ V}$
$v_7 = 3 \text{ V}$

The branch currents are found by applying the constitutive laws:

$$\begin{aligned}
 i_1 &= v_1 / R_1 = -2 \text{ A} \\
 i_2 &= v_2 / R_2 = 3 \text{ A} \\
 i_3 &= v_3 / R_3 = 1 \text{ A} \\
 i_4 &= v_4 / R_4 = 2 \text{ A} \\
 i_5 &= v_5 / R_5 = -3 \text{ A} \\
 i_6 &= I_6 = 5 \text{ A}
 \end{aligned}$$

Note that the constitutive law for the voltage source,

$v_7 = V_7$, for all i_7 gives no information about i_7 . To find i_7 , apply KCL at the V_7 node:

$$i_7 + i_1 = 0$$

$$\Rightarrow \boxed{i_7 = +2 \text{ A}}$$

2. Find the net power dissipated by the circuit:

$$\begin{aligned}
 P &= \sum_n i_n v_n \\
 &= (-2)(-6) + (3)(6) + (1)(3) + (2)(6) + (-3)(-3) \\
 &\quad + (5)(-12) + (2)(3)
 \end{aligned}$$

$$\Rightarrow P = 12 + 18 + 3 + 12 + 9 - 60 + 6 = 0 \text{ W}$$

$$P = 0 \text{ W}$$

Note that the current source supplies power (-60 W), and the voltage source absorbs power (+6 W).