

**Massachusetts Institute of Technology**  
**Department of Electrical Engineering and Computer Science**  
6.061 Introduction to Power Systems

Problem Set 2 Solutions

February 16, 2003

**Problem 1:** 1. The switch is *opened* at time  $t = 0$ , and the current source has a constant current  $I_0 = 10A$ . The *particular* solution is  $V_p = 0$ . Noting that the homogeneous equation is:

$$\frac{L}{R} \frac{dv_0}{dt} + v_0 = 0$$

which is solved by:

$$v_0 = V_H e^{-\frac{L}{R}t}$$

The initial condition is simply:

$$V_H = RI_0 = 10A \times 100\Omega = 1,000V$$

So that the total solution is

$$v_0 = 1000e^{-1000t}$$

2. The source is changed to be  $i_s = 10\cos\omega t$  with  $\omega = 2\pi \times 60Hz$ . The *particular* solution is the sinusoidal steady state solution to

$$i_L + \frac{v_0}{R} = I_s = i_L + \frac{L}{R} \frac{di_L}{dt} = \text{Re}\{|I_s| \cos\omega t\}$$

That solution is simply:

$$i_L = \text{Re}\{\underline{I}_L e^{j\omega t}\}$$

where

$$\underline{I}_L = \frac{I_s}{1 + j\omega \frac{L}{R}}$$

So then the *particular* solution for inductor current is

$$i_{Lp} = \frac{I_s}{\sqrt{1 + \left(\frac{\omega L}{R}\right)^2}} \cos\omega t - \phi$$

where the phase angle is  $\phi = \tan^{-1} \frac{\omega L}{R}$ . The whole solution is

$$v_o = V_H e^{-\frac{R}{L}t} + I_s (\cos\omega t - \cos(\omega t - \phi))$$

Since the same initial condition as in the first part of the problem holds, the full solution is:

$$v_o = RI_s \left( \cos\phi e^{-\frac{R}{L}t} + \cos\omega t - \cos(\omega t - \phi) \right)$$

3. **For 6.979** Here is a script which calculates and plots the results derived here and which does the simulation too:

```

\% PS2 Problem 1
R=100;
L=.1;
t = 0:.000001:.01;
V1 = 1000 .* exp(-(R/L) .* t);
I10 = 0;
[ts, I1] = ode23('isubs', t, I10);
Vs1 = R .* (10 - I1);
figure(1)
plot(t, V1, ts, Vs1);
om = 2*pi*60;
phi = atan(om*L/R);
t2 = 0:.000001:.05;
Is = 10;
I1p = (Is/sqrt(1+(om*L/R)^2)) .* cos(om .* t2 - phi);
V2 = R*Is*cos(phi) .* exp(-(R/L) .* t2) + R*Is.* cos(om .* t2) - R .* I1p;
[tss, I12] = ode45('isubs2', t2, I10);
V2s = R .* (Is .* cos(om .* tss) - I12);
figure(2)
plot(t2, V2, tss, V2s);

```

Below are the two subroutines called by ode23:

```

function didt = isubs(t, i)
R = 100;
L=.1;
Is = 10;
didt = R*(Is-i)/L;
-----
function didt = isubs2(t, i)
R = 100;
L=.1;
om = 2*pi*60;
Is = 10*cos(om*t);
didt = R*(Is-i)/L;
-----

```

### Problem 2: 'Buck converter'

1. The *average* output voltage is simply

$$\langle v_o \rangle = dV_s$$

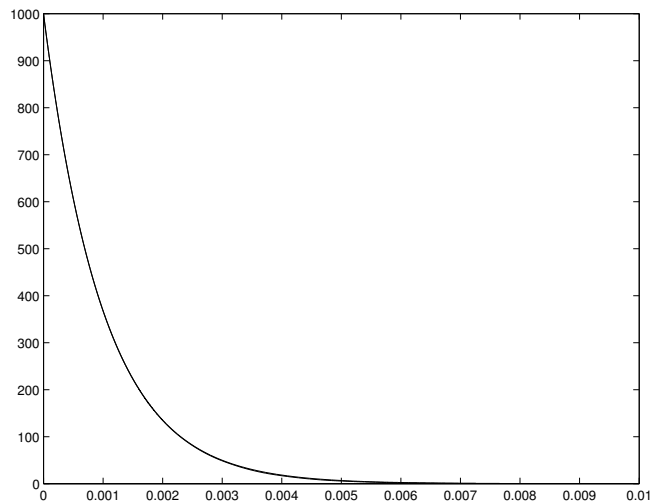


Figure 1: Solution to Problem 1, part 1

2. We know the maximum current (in steady state) is

$$i_m = \frac{V_s}{R} \frac{1 - e^{-\frac{R}{L}t_{on}}}{1 - e^{-\frac{R}{L}T}}$$

where  $t_{on} = dT$  and of course the minimum current is:

$$i_l = i_m e^{-\frac{R}{L}t_{off}}$$

and of course  $t_{off} = (1 - d)T$  This little script here calculates and plots the ripple for the full range of duty cycle and prints the value for a duty cycle of 1/2.:

```

R = 10;
L = .02;
T = 1e-4;
dc = .5;
ton = T*dc;
toff = T*(1-dc);
Vs = 100;
Vm = Vs *(1-exp(-(R/L)*ton))/(1-exp(-(R/L)*T));
Vl = Vm * exp(-(R/L)*toff);
Vr = Vm-Vl;
fprintf('50 percent duty cycle\n');
fprintf('Max Voltage = %g\n',Vm);
fprintf('Min Voltage = %g\n',Vl);
fprintf('Ripple Voltage = %g\n',Vr);
d = 0:.01:1;
t_on = T .* d;
t_off = T .* (1-d);
Vm = Vs .* (1-exp(-(R/L) .* t_on)) ./ (1-exp(-(R/L)*T));

```

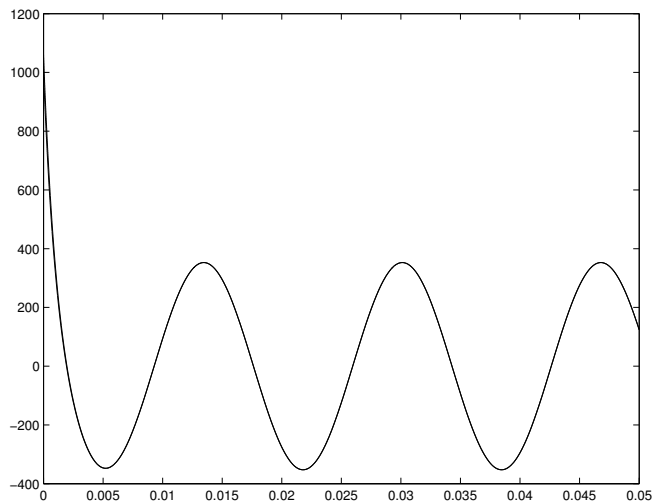


Figure 2: Solution to Problem 1, part 2

```
Vl = Vm .* exp(-(R/L) .*t_off);
Vr = Vm-Vl;
figure(3)
plot(d, Vr)
title('Problem Set 2, Problem 2')
ylabel('Ripple Voltage');
xlabel('Duty Cycle')
```

-----  
Here is the output for 50\%:

```
>> p2
50 percent duty cycle
Max Voltage = 50.625
Min Voltage = 49.375
Ripple Voltage = 1.24993
```

3. Simulation: Here is a script which does the simulation. Note that this repeats a few cycles at the end to get a better idea of steady state operation. These may be compared with the numbers obtained above

```
-----
% Problem set 2, PROblem 2 simulation
% buck converter
global Vs L R
Vs=100;
L=.02;
R=10;
il=[];
t = [];
T = 1e-4;
```

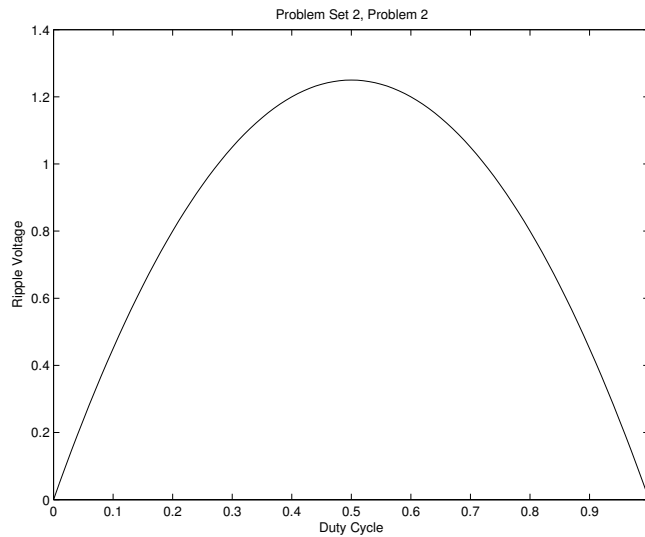


Figure 3: Buck Converter Ripple vs. duty cycle

```

d = .5;
ton = T*d;
toff = T*(1-d);
S0=0;
for n = 0:100
    [tt, S] = ode23('bon', [n*T n*T+ton], S0);
    t = [t' tt']';
    il = [il S'];
    S0 = S(length(tt));
    [tt, S] = ode23('boff', [n*T+toff (n+1)*T], S0);
    t = [t' tt']';
    il = [il S'];
    S0 = S(length(tt));
end
vo = R .* il;
figure
plot(t, vo)
title('Buck Converter Simulation')
ylabel('Volts');
xlabel('Time, sec');
% now just to get the last few cycles
tf = [];
ilf = [];
for n = 100:102
    [tt, S] = ode23('bon', [n*T n*T+ton], S0);
    tf = [tf' tt']';
    ilf = [ilf S'];
    S0 = S(length(tt));

```

```

[tt, S] = ode23('boff', [n*T+toff (n+1)*T], S0);
tf = [tf' tt']';
ilf = [ilf S'];
S0 = S(length(tt));
end
vof = R*ilf;
figure
plot(tf, vof)
title('Buck Converter Simulation')
ylabel('Volts');
xlabel('Time, sec');
-----
function DS = bon(t, il)
global Vs L R
DS = (Vs - R*il)/L;
-----
function DS = boff(t, il)
global Vs L R
DS = (- R*il)/L;
-----

```

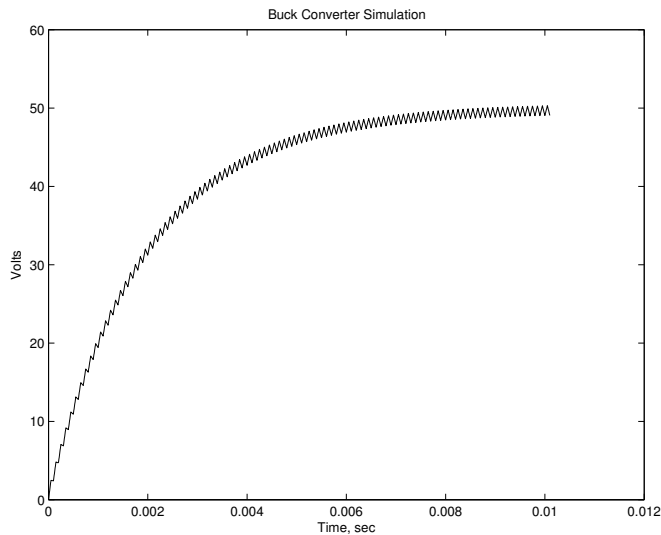


Figure 4: Buck Converter Voltage Buildup

**Problem 3:** This problem has two loops and two energy storage elements. The two loop equations are:

$$L \frac{di_L}{dt} + Ri_L - RC \frac{dv_c}{dt} = V_s$$

$$2RC \frac{dv_c}{dt} + v_c - Ri_L = 0$$

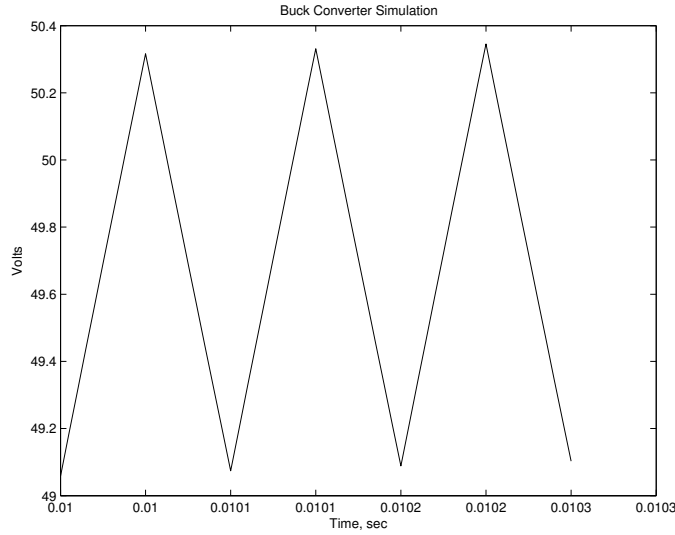


Figure 5: Buck Converter in Steady State

Now by multiplying the second of these by  $1/2$  and adding it to the first, we get a separated set of state equations which we can solve directly and use in a simulation:

$$\begin{aligned} V_s &= L \frac{di_L}{dt} + \frac{R}{2} i_L + \frac{1}{2} v_c \\ 0 &= 2RC \frac{dv_c}{dt} + v_c - R i_L \end{aligned}$$

The characteristic equation for this is the determinant of:

$$\begin{bmatrix} SL + \frac{R}{2} & \frac{1}{2} \\ -R & 2RCS + 1 \end{bmatrix} \begin{bmatrix} i_L \\ v_c \end{bmatrix} = \begin{bmatrix} V_s \\ 0 \end{bmatrix}$$

which is

$$\left( SL + \frac{R}{2} \right) (2RCS + 1) + \frac{R}{2} = 0$$

or

$$S^2 + S \left( \frac{1}{2RC} + \frac{R}{2L} \right) + \frac{1}{2LC} = 0$$

which is solved by

$$S = -\alpha \pm j\omega$$

where

$$\begin{aligned} \alpha &= \frac{1}{2} \left( \frac{1}{2RC} + \frac{R}{2L} \right) \\ \omega &= \sqrt{\frac{1}{2LC} - \alpha^2} \end{aligned}$$

It is clear that the particular solution to this problem is  $v_P = 0$  (note that the excitation is DC and the output is in series with a capacitor). So the whole solution must be:

$$v_o = Ae^{(-\alpha+j\omega)t} + Be^{(-\alpha-j\omega)t}$$

Noting the inductor in series with the source, we can see that the voltage at  $t = 0+ = 0$ , or  $A + B = 0$ .

The *time derivative* of output voltage at  $t = 0+$  is:

$$\frac{dv_o}{dt} = \frac{1}{2} \frac{R}{L} V_s = 2j\omega A$$

so that whole solution is simply:

$$v_o = \frac{V_s R}{2 L \omega} e^{-\alpha t} \sin \omega t$$

Here is a script which simulates this and which plots both the simulated and analytical solutions. Note they plot right on top of each other:

```

\% Problem Set 2, Problem 3
global Vs R L C
Vs = 100;
R = 10;
L = .001;
C = 1e-5;
alf = 1/(4*R*C)+R/(4*L);
om = sqrt(1/(2*L*C)-alf^2);
Vm = .5*(Vs/om)*(R/L);
t=0:5e-6:2e-3;
Vo = Vm .* exp(-alf .* t) .* sin(om .* t);
[ts X] = ode23('rlcsim', t, [0 0]');
i_L = X(:,1);
v_c = X(:,2);
V_o = .5*R .* i_L - .5 .* v_c;
figure
plot(t, Vo, ts, V_o)
title('Problem Set 2, Problem 3')
ylabel('Volts')
xlabel('Seconds');
-----
function xdot = rlcsim(t, X);
global Vs R L C
il = X(1);
vc = X(2);
didt = (Vs - .5*R*il - .5*vc)/L;
dvdt = (R*il-vc)/(2*R*C);
xdot = [didt dvdt]';
-----

```



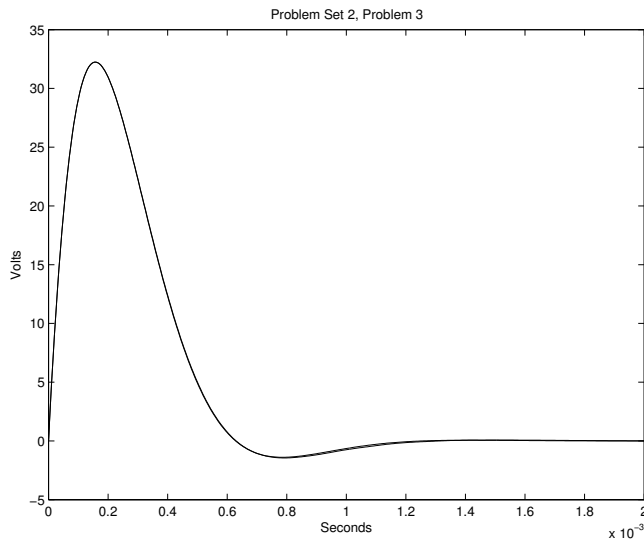


Figure 6: Solution for Problem 3: Analytic and Simulated

**Problem 4: for 6.979** This one is much easier than it looks!

Note that there are two periods of time. First, when the switch is ON (for 10 mS) the diode is back-biased and inductor current is simply:

$$i_L = \frac{V}{L}t$$

With a drive voltage of 100 volts and an inductance of 100 mHy, the rate of change of current in the inductance is  $\frac{V}{L} = 1000A/sec$ . After 10 mS the inductor current is 10 A.

As the switch is opened current circulates through the capacitance and diode. At first it looks like a simple harmonic oscillator with  $i_L = I_0 \cos \omega t$ . The frequency of oscillation is  $\omega = \frac{1}{\sqrt{LC}} = 1000rad/sec$ . Now, note that this can keep up only for 1/4 of a cycle, or until the current tries to reverse. The diode becomes forward biased and the voltage on the capacitance becomes steady. That voltage is:

$$V_c = -\frac{1}{C} \int_0^{\frac{\pi}{2\omega}} I_0 \cos \omega t dt = -\frac{I_0}{\omega C} = -I_0 \sqrt{\frac{L}{C}}$$

Since the current  $I_0$  is 10 A and  $\sqrt{\frac{L}{C}} = 100\Omega$ , the final output voltage is 1000 V.