

**Massachusetts Institute of Technology**  
**Department of Electrical Engineering and Computer Science**  
 6.061 Introduction to Power Systems

Problem Set 3 Solutions

February 17, 2003

**Problem 1:** Assuming that sending-end and receiving end voltages are of equal magnitude and differ in phase angle by  $\delta$ , *real* power flow is

$$P = \frac{|V|^2}{X_L} \sin \delta$$

or, in terms of the values given in the problem:

$$10 \times 10^6 = \frac{(10 \times 10^3)^2}{5} \times \sin \delta$$

Which implies that  $\sin \delta = \frac{1}{2}$ , or  $\delta = 0.5236 \text{ Radians} = 30^\circ$ . Figure 2 below shows, approximately, the phasor diagram that results.

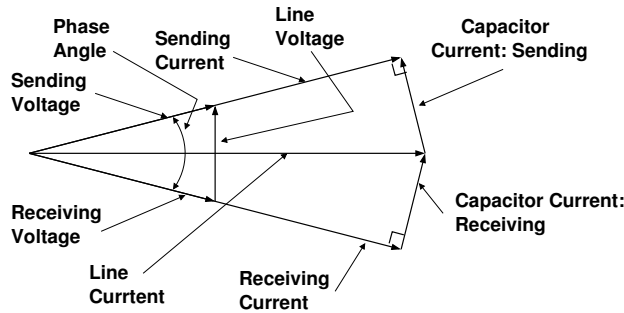


Figure 1: Transmission Line

Voltage across the transmission line is

$$V_L = 2|V| \sin \frac{\delta}{2} = 5176V$$

Reactive power absorbed by the line is

$$Q_L = \frac{|V_L|^2}{X_L} = 5.359 \text{ MVAR}$$

Reactive power required of the capacitance at each end is half of this, so that

$$Q_C = \frac{1}{2} Q_L = \frac{|V|^2}{X_C} = |V|^2 \omega C$$

Or:

$$C = \frac{Q_L}{2\omega|V|^2} \approx 71 \mu F$$

**Problem 2:** As seen from the source, line plus load impedance are

$$Z = j\omega L + R$$

Since  $\omega L = 377 \times .0265 \approx 10\Omega$ , the total impedance has magnitude of  $75.66\Omega$  and a phase angle of very nearly  $7.6^\circ$

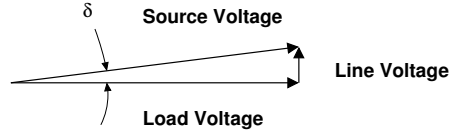


Figure 2: Phasor Diagram for Problem 2

Load current is

$$|I_L| = \frac{8000}{75.66} \approx 105.7A$$

and power in the load is

$$P_L = |I_L|^2 R \approx 838.4kW$$

For the second part, including the parallel capacitance, we may write the expression for load voltage, a simple voltage divider:

$$V_L = V_S \frac{R \parallel \frac{1}{j\omega C}}{R \parallel \frac{1}{j\omega C} + j\omega L} = \frac{V_S}{(1 - \omega^2 LC) + j\omega \frac{L}{R}}$$

To make  $V_L = V_S$  we need to make

$$\left(1 - \omega^2 LC\right)^2 + \left(\omega \frac{L}{R}\right)^2 = 1$$

Which, after a little algebra, boils to

$$\omega C = \frac{1}{\omega L} \pm \sqrt{\left(\frac{1}{\omega L}\right)^2 - \left(\frac{1}{R}\right)^2}$$

The smaller capacitance results from taking the minus sign, for which the value of  $C \approx 2.37\mu F$ .

It is possible to solve, using MATLAB, the magnitude of receiving end voltage vs. capacitance (shown in Figure 1).

**Problem 3:** If the capacitor is really holding voltage constant, maximum and minimum currents in the inductor are:

$$\begin{aligned} I_m &= I_\ell + \frac{V_s - V_o}{L} t_{on} \\ I_\ell &= I_m - \frac{V_o}{L} t_{off} \end{aligned}$$

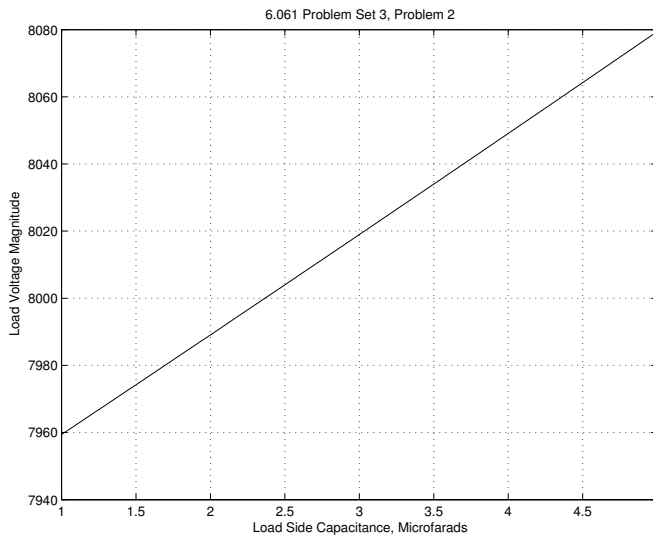


Figure 3: Receiving End Voltage vs. Compensating Cap

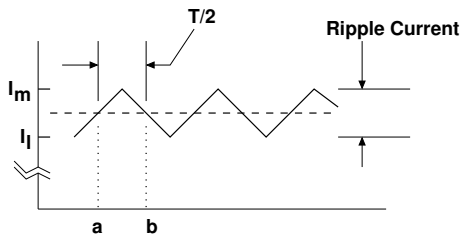


Figure 4: Cartoon of ripple current

which may be handily solved for, as expected:

$$V_o = V_s \frac{t_{on}}{t_{on} + t_{off}}$$

Now, if output voltage is indeed constant, we may also conclude that average inductor current is the same as output current:

$$\frac{I_\ell + I_m}{2} = \frac{V_o}{R}$$

Combining these relationships we find:

$$I_m = \frac{V_o}{R} + \frac{1}{2} \frac{V_o}{L} t_{off} = 5.625 A$$

$$I_\ell = \frac{V_o}{R} = \frac{1}{2} \frac{V_o}{L} t_{off} = 4.375 A$$

Now, to get ripple voltage, note that the area of current ripple as shown in Figure 4 (the area above the average current line) represents charge added to the capacitor during the positive ripple excursion. This is:

$$\Delta Q = \frac{1}{2} \Delta I \frac{T}{2} = \frac{1}{2} \times \frac{1}{2} \times 10^{-4} \times .625 A \approx 1.56 \times 10^{-5} \text{ coulombs}$$

With  $C = 100\mu F$ , this implies a voltage excursion of about 156 mV.

The script for simulating this circuit is appended. What it does is shown in Figure 5, which shows voltage buildup and Figure 6 which shows a couple of cycles near steady state to show ripple.

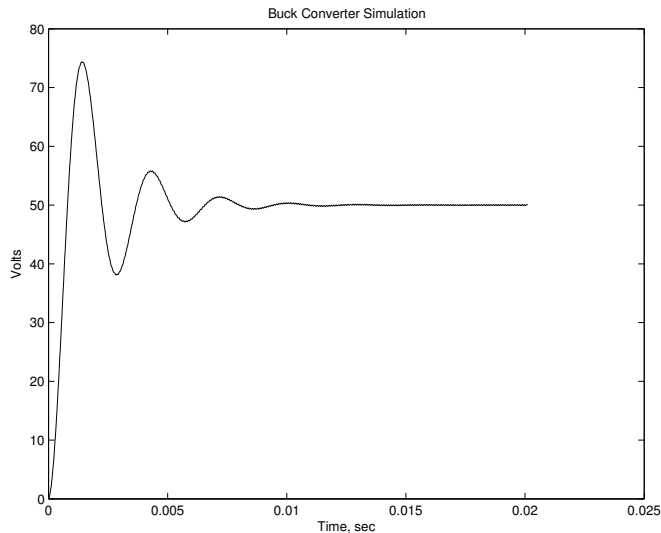


Figure 5: Voltage Buildup in Capacitor Filtered Buck Converter

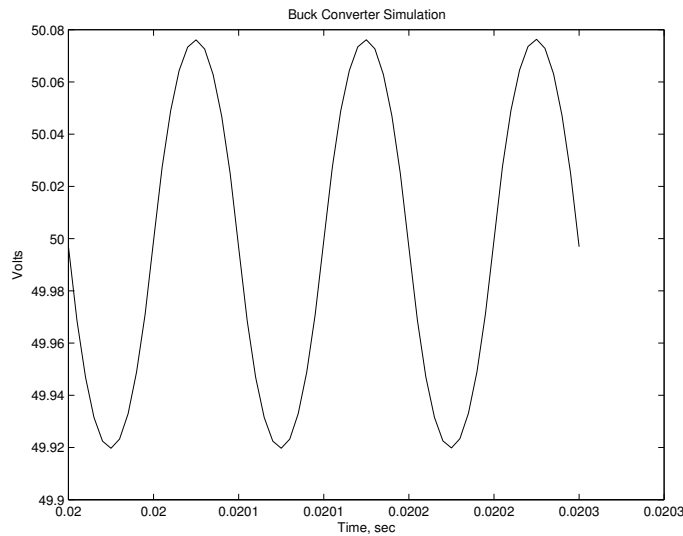


Figure 6: Ripple in Capacitor Filtered Buck Converter

**Problem 4:** In the Boost Converter, with  $t_{on} = t_{off}$ , output voltage should be just twice input voltage, or 100 V. With a load of  $10\Omega$ , this would draw 10 A. Voltage change is then:

$$\Delta V = \frac{I t_{off}}{C}$$

which, for 10 A,  $t_{off} = \frac{1}{2} \times 10^{-4}$  seconds and  $C = 10^{-4}$  F, is just about 5 V.

This circuit, too, has been simulated, and the scripts are appended. The results are shown in Figure 7 (voltage buildup) and Figure 8 (steady state ripple).

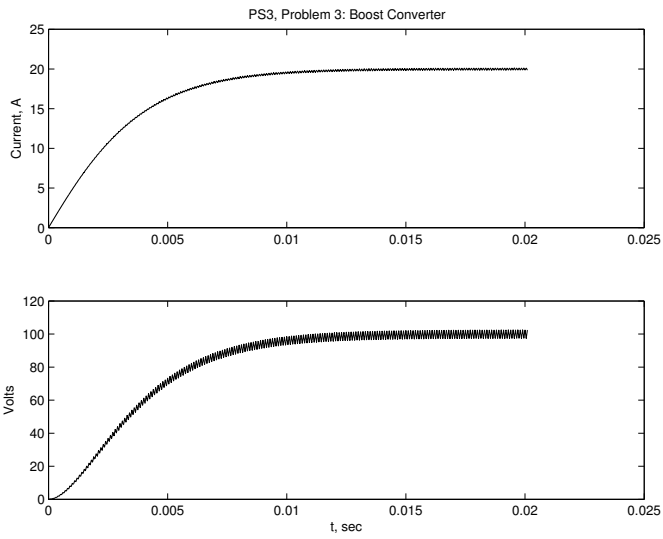


Figure 7: Boost Converter Voltage Buildup

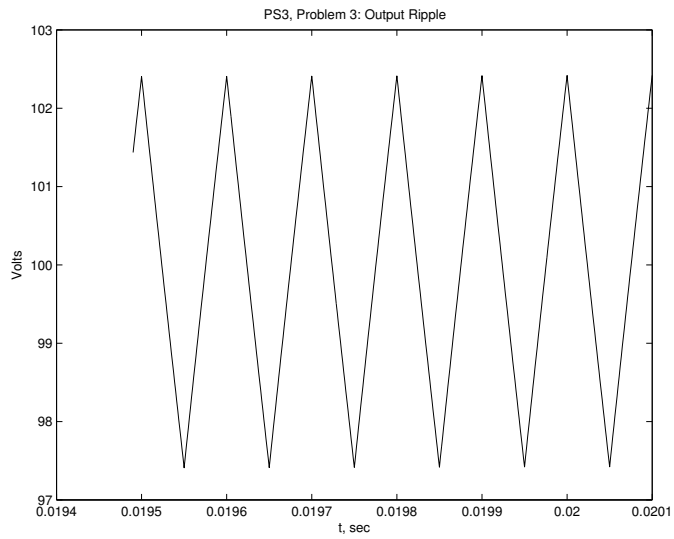


Figure 8: Boost Converter Voltage Ripple

Here are the buck and boost converter scripts:

```
-----  
% Problem set 3, PProblem 3 simulation  
% buck converter with output capacitor  
global Vs L R C  
Vs=100;  
L=.002;  
R=10;  
C=100e-6;  
X=[];  
t = [];  
T = 1e-4;  
d = .5;  
ton = T*d;  
toff = T*(1-d);  
S0=[0; 0];  
for n = 0:200  
    [tt, S] = ode23('bon', [n*T n*T+ton], S0);  
    t = [t' tt']';  
    X = [X S'];  
    S0 = S(length(tt),:);  
    [tt, S] = ode23('boff', [n*T+toff (n+1)*T], S0);  
    t = [t' tt']';  
    X = [X S'];  
    S0 = S(length(tt),:);  
end  
I1 = X(1,:);  
vo = X(2,:);  
figure(1)  
plot(t, vo)  
title('Buck Converter Simulation')  
ylabel('Volts');  
xlabel('Time, sec');  
% now just a couple of cycles to get ripple  
tf = [];  
Xf = [];  
for n = 200:202  
    [tt, S] = ode23('bon', [n*T n*T+ton], S0);  
    tf = [tf' tt']';  
    Xf = [Xf S'];  
    S0 = S(length(tt),:);  
    [tt, S] = ode23('boff', [n*T+toff (n+1)*T], S0);  
    tf = [tf' tt']';  
    Xf = [Xf S'];  
    S0 = S(length(tt),:);  
end
```

```
end
Ilf = Xf(1,:);
vof = Xf(2,:);
figure(2)
plot(tf, vof)
title('Buck Converter Simulation')
ylabel('Volts');
xlabel('Time, sec');
```

```
-----
function DS = bon(t, X)
global Vs L R C
il = X(1);
vc = X(2);
didt = (Vs-vc)/L;
dvdt = (il-vc/R)/C;
DS = [didt dvdt]';
```

```
-----
function DS = boff(t, X)
global Vs L R C
il = X(1);
vc = X(2);
didt = -vc/L;
dvdt = (il-vc/R)/C;
DS = [didt dvdt]';
-----
```

```

-----
% trivial boost converter model
global vs L C R
vs = 50;
f = 10000;
alf = .5;
L = 10e-3;
C = 100e-6;
R = 10;
T=1/f;
Dton = alf/f;
Dtoff = (1-alf)/f;
dton = Dton/10;
dtoff = Dtoff/10;
v0 = 0;
i0 = 0;
t = [];
i = [];
v = [];
for n = 0:200;
[tc, S] = ode45('upon',[n*T n*T+Dton] , [i0 v0]');
t = [t tc'];
ic = S(:,1);
vc = S(:,2);
i = [i ic'];
v = [v vc'];
i0 = ic(length(tc));
v0 = vc(length(tc));
[tc, S] = ode45('upoff',[n*T+Dton (n+1)*T] , [i0 v0]);
ic = S(:,1);
vc = S(:,2);
t = [t tc'];
i = [i ic'];
v = [v vc'];
i0 = ic(length(tc));
v0 = vc(length(tc));
end
figure(1)
subplot 211
plot(t, i)
title('PS3, Problem 3: Boost Converter')
ylabel('Current, A');
subplot 212
plot(t, v)
ylabel('Volts');

```



```

xlabel('t, sec');
N = length(t);
figure(2)
plot(t(N-500:N), v(N-500:N))
title('PS3, Problem 3: Output Ripple')
ylabel('Volts');
xlabel('t, sec');

```

```

-----
function Sdot = up(t, S)
global vs L C R
    il = S(1);
    vc = S(2);
    vdot = (1/C) * ( - vc/R);
    idot = (1/L) * (vs);
    Sdot = [idot vdot]';

```

```

-----
function Sdot = up(t, S)
global vs L C R
    il = S(1);
    vc = S(2);
    vdot = (1/C) * (il - vc/R);
    idot = (1/L) * (vs - vc);
    Sdot = [idot vdot]';

```