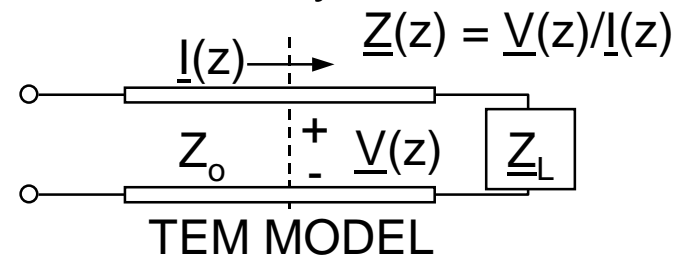


CIRCUIT TRANSFORMATION MAGIC

Printed Microwave Circuits (TEM lines):

- Can contain R's (resistive rectangles)
- Can yield L's and C's (near ω_0)
- Can be resonators for tuning or transformer use
- Can match impedances to maximize power transfer
- Can perform nearly all circuit functions with transistors only
- Has size scale $\sim \lambda/4 \Rightarrow f \gtrsim 1$ GHz



Waveguide Circuits and Systems:

- Can be made lossy
- Can have inductive or capacitive obstacles (L's and C's)
- Can resonate for tuning or transforming
- Can match impedances to maximize power transfer
- Can make circulators (non-reciprocal devices)

Optical Circuits:

Similar to waveguide circuits, but in fibers or free space

GAMMA PLANE \Leftrightarrow SMITH CHART

TEM Lines:

$$\underline{V}(z) = \underline{V}_+ e^{-jkz} + \underline{V}_- e^{+jkz}$$

$$\underline{I}(z) = Y_0 \left[\underline{V}_+ e^{-jkz} - \underline{V}_- e^{+jkz} \right]$$

$$\underline{Z}(z) = Z_0 (1 + \underline{\Gamma}(z)) / (1 - \underline{\Gamma}(z))$$

$$\underline{\Gamma}(z) \triangleq (\underline{V}_- / \underline{V}_+) e^{2jkz} = \underline{\Gamma}_L e^{2jkz}$$


$$\underline{Z}_n = \underline{Z}(z) / Z_0 = R_n + jX_n:$$

Gamma plane is useful because $\underline{\Gamma}(z) = \underline{\Gamma}_L e^{2jkz}$, which is simply rotation on the plane.

One-to-One Mapping:

$$\underline{Z}_n = (1 + \underline{\Gamma}) / (1 - \underline{\Gamma})$$
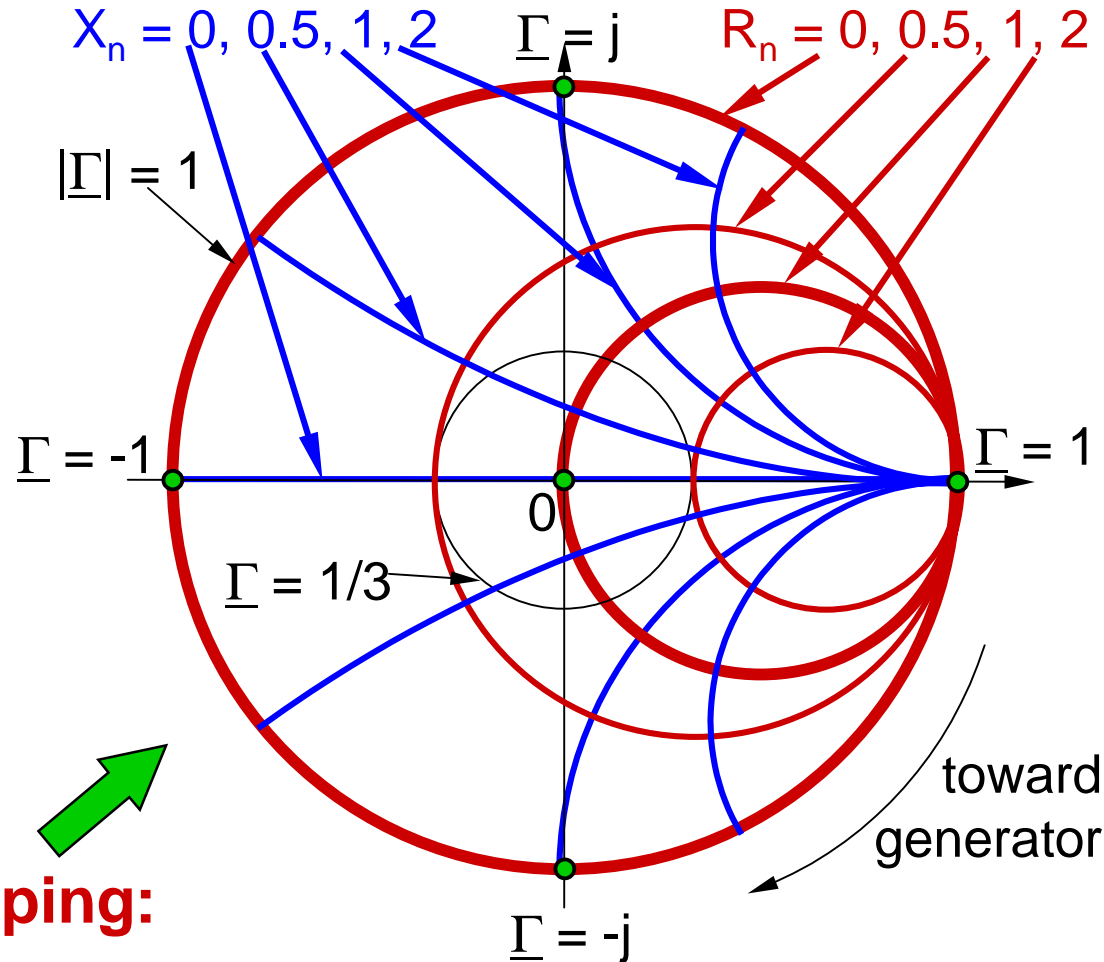
$$\underline{\Gamma} = (\underline{Z}_n - 1) / (\underline{Z}_n + 1)$$



SPECIAL PROPERTIES OF THE SMITH CHART

Admittance \Leftrightarrow Impedance:

$$\text{If } \underline{Z}_n \rightarrow \underline{Z}_n^{-1} = \underline{Y}_n, \text{ then } \underline{\Gamma} \rightarrow \underline{\Gamma}^*$$

Proof: $\underline{\Gamma} = (\underline{Z}_n - 1)/(\underline{Z}_n + 1)$, so if $\underline{Z}_n \rightarrow \underline{Z}_n^{-1}$, then

$$(\underline{Z}_n^{-1} - 1)/(\underline{Z}_n^{-1} + 1) = (1 - \underline{Z}_n)/(\underline{Z}_n + 1) = -\underline{\Gamma} \quad \text{Q.E.D.}$$

Voltage Standing Wave Ratio (VSWR):

$$\begin{aligned} \text{VSWR} &= |\underline{V}_{\max}|/|\underline{V}_{\min}| = \left(\left| \underline{V}_+ e^{-jkz} \right| + \left| \underline{V}_- e^{+jkz} \right| \right) / \left(\left| \underline{V}_+ e^{-jkz} \right| - \left| \underline{V}_- e^{+jkz} \right| \right) \\ &= (1 + |\underline{\Gamma}|)/(1 - |\underline{\Gamma}|) = R_n \max \quad (\text{evident on Chart, on x axis}) \end{aligned}$$


Rotation Around Chart:

$\lambda/2$ corresponds to one full rotation around chart



$$\left(e^{2jkz} \Rightarrow e^{2j(2\pi/\lambda)(\lambda/2)} = e^{j2\pi} = 1 \right)$$

MATCHING IMPEDANCES

Problem: Losslessly Match Given Load:

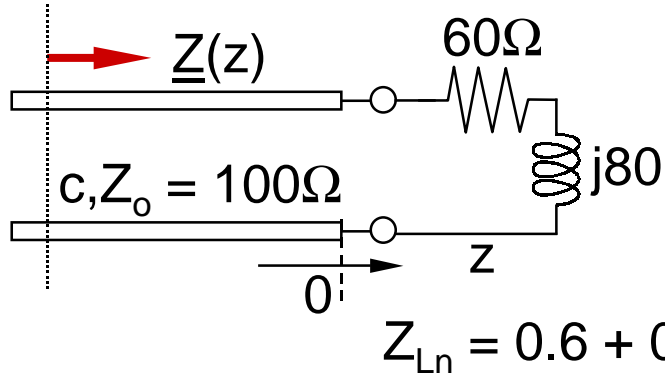

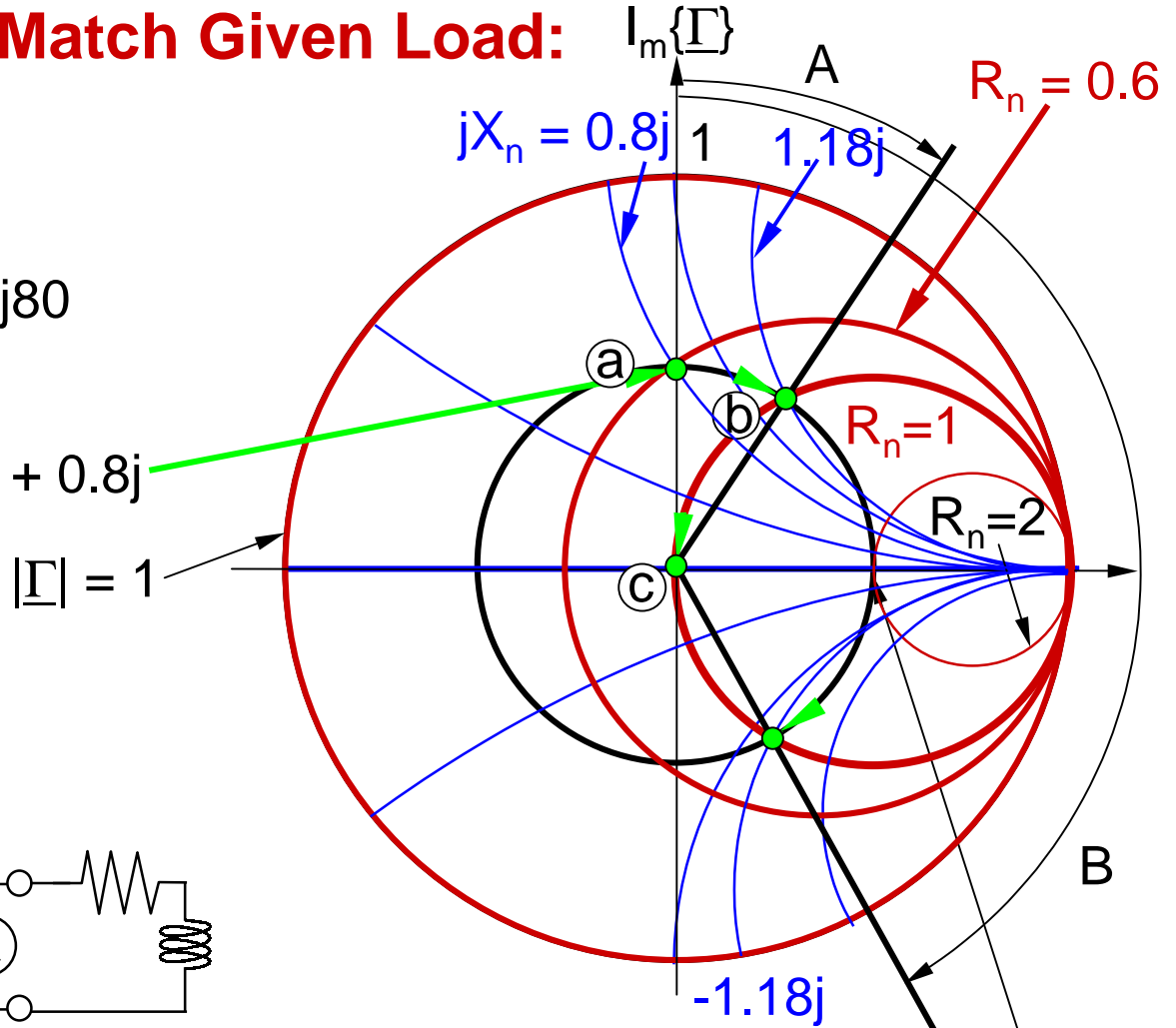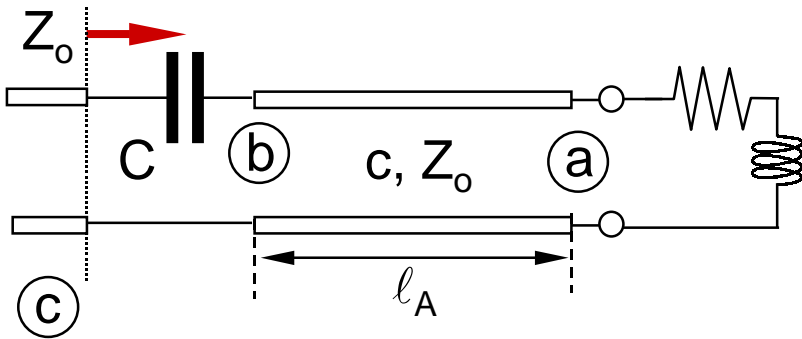$jX = -j1.18Z_0 = 1/j\omega C$
 So $C = 1/118\omega$




(Or use $j\omega L = j1.18Z_0$ and l_B)



(Since $R_{n\max} = 2$, so is the VSWR for the mismatched load)

MATCHING ADMITTANCES

Reactive Tuning Elements in Parallel:

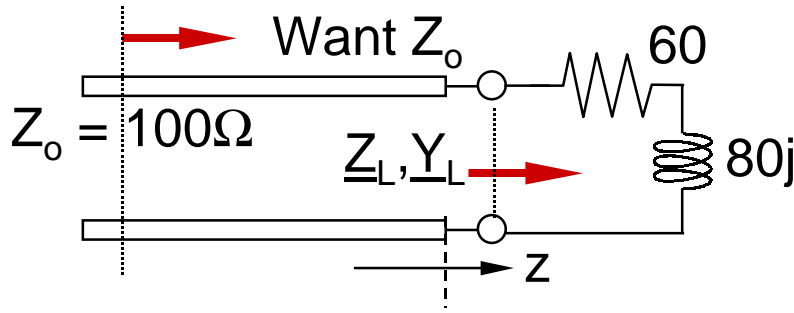

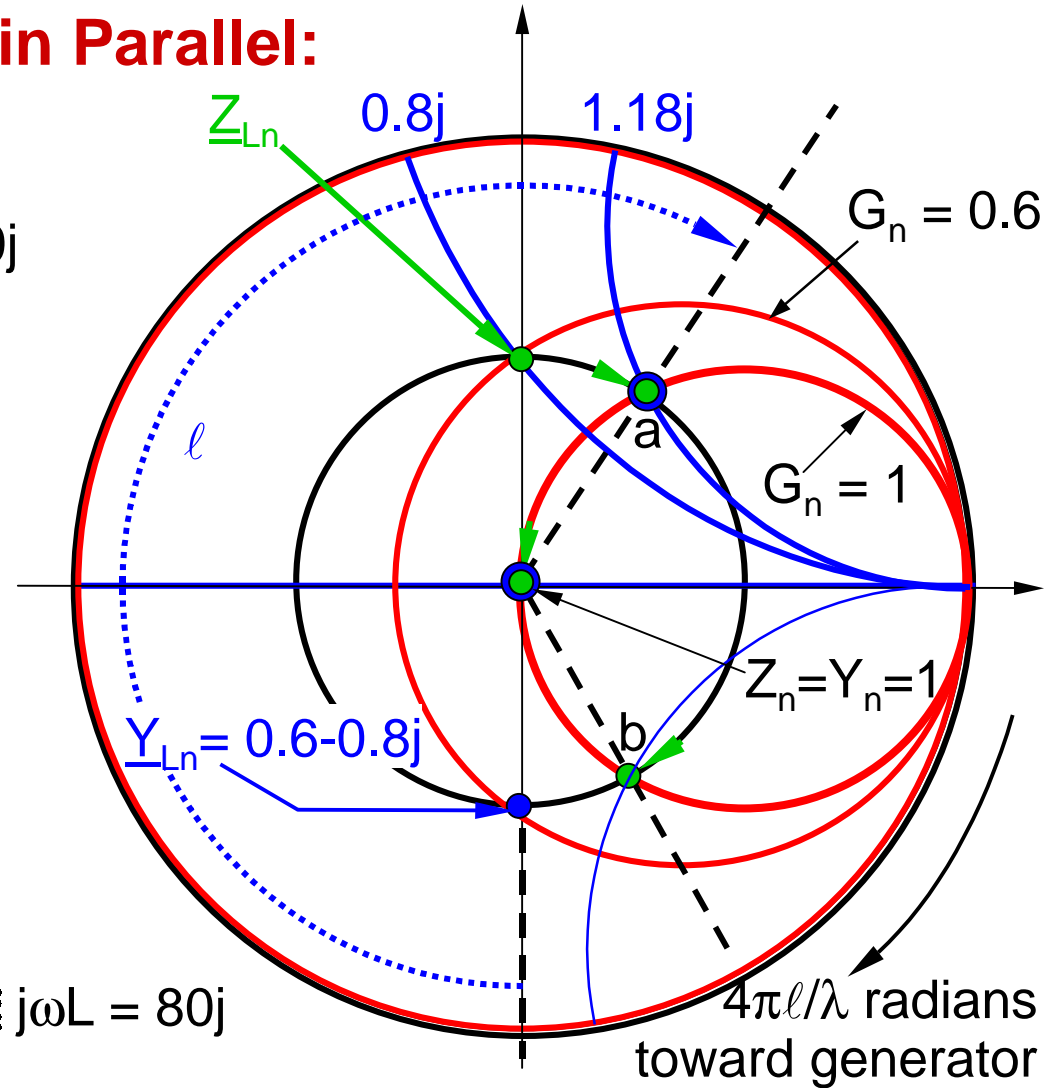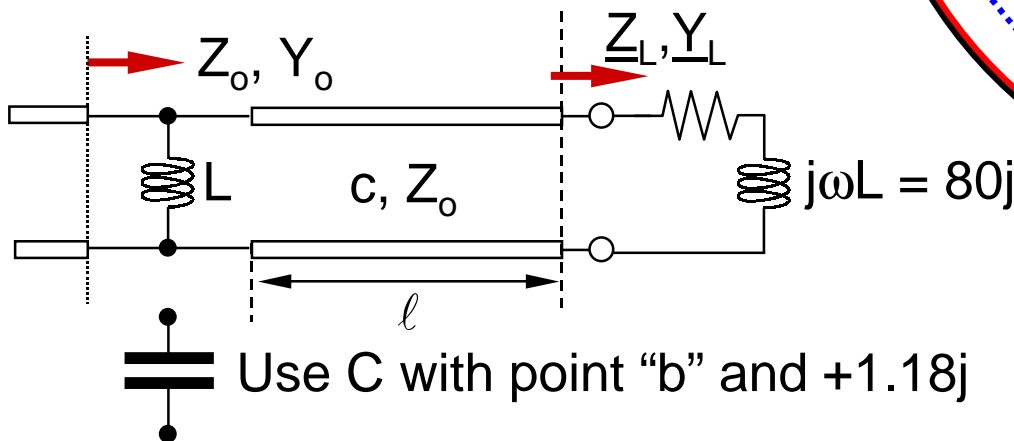Find Z_{Ln} on chart, then Y_{Ln} opposite; rotate l to "a"
 where $G_n = 1$ and add $-1.18j$
 admittance to yield $Y_n = Y_o$
 $Y = -1.18jY_o = 1/j\omega L$
 $\Rightarrow L = Z_o/1.18\omega$




Can match any load!
 (beware resonances)


QUARTER-WAVE TRANSFORMER

Matching Real Impedances without L,C:

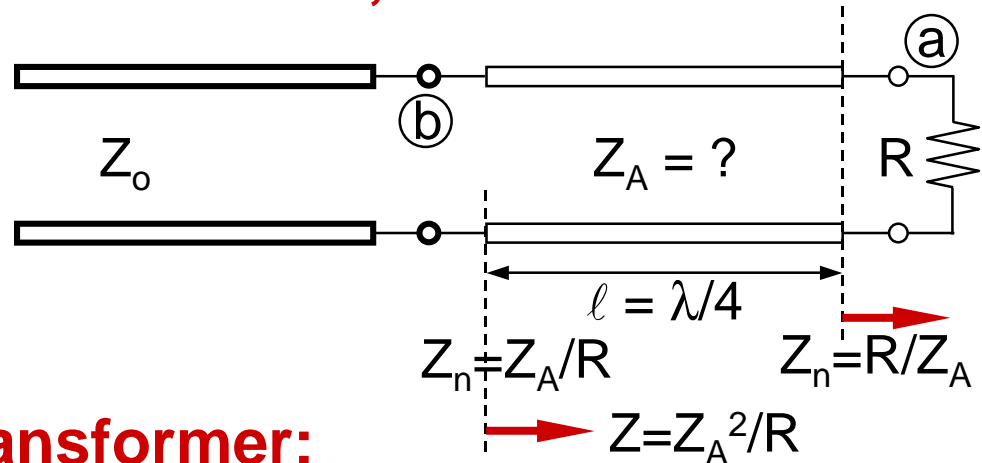Let: $l = \lambda/4$, then
 Setting: $Z_o = Z_A^2/R$,
 Yields: $Z_A = (Z_o R)^{0.5}$



Optical Quarter-Wave Transformer:

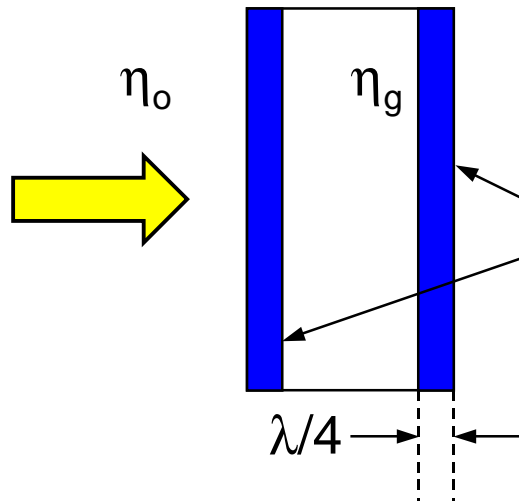

$$\eta_o = (\mu_o/\epsilon_o)^{0.5} = 377\Omega$$

$$\eta_t = (\eta_o \eta_g)^{0.5} \Rightarrow \epsilon_t = (\epsilon_o \epsilon_g)^{0.5}$$

Applications: coated camera lenses, glasses, optoelectronic components, high-power lasers, etc.


Invented by Prof. Smakula at Leitz

MORE QUARTER-WAVE TRANSFORMERS

Waveguide Transformers:


Z_0 varies with waveguide sizes

$$Z_t = (Z_a Z_b)^{0.5}$$

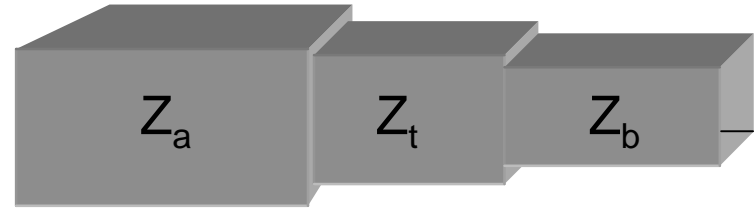

Multi-step Transitions:

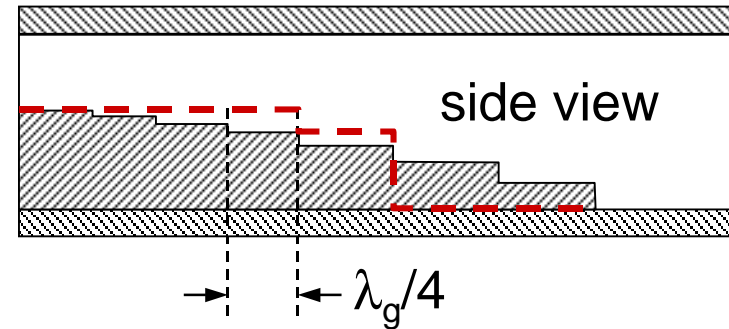Waveguides can have N multiple steps spaced $\lambda/4$ apart




Example, 1:256 Transformer:

For $N = 2$, $Z_a = 1$ ohm, $Z_b = 256$ ohms, and $Z_t = (1 \times 256)^{0.5} = 16$ ohms

For $N = 4$, $Z_{t1} = (1 \times 16)^{0.5} = 4$ ohms, $Z_{t2} = 16$, $Z_{t3} = (16 \times 256)^{0.5} = 64$

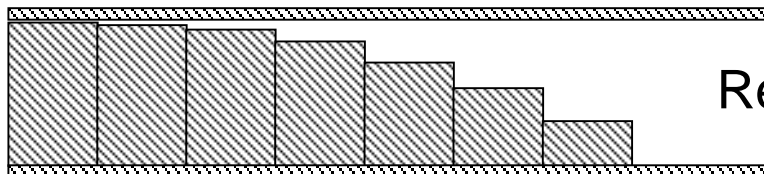For $N = 8$, $Z_{t1} = (1 \times 4)^{0.5} = 2$, $Z_{t2} = 4$, (rest are 8, 16, 32, 64, and 128 ohms)



Result is exponential series


EXPONENTIAL TRANSITIONS AND HORNS

Acoustic Transformers, Exponential Horns:

We use $N \cong 4L/\lambda_g$ sections, where L is the length of the transformer
In the limit we can smooth the steps to yield an exponential shape

Acoustic Examples:

French horn, trumpet, loudspeakers:

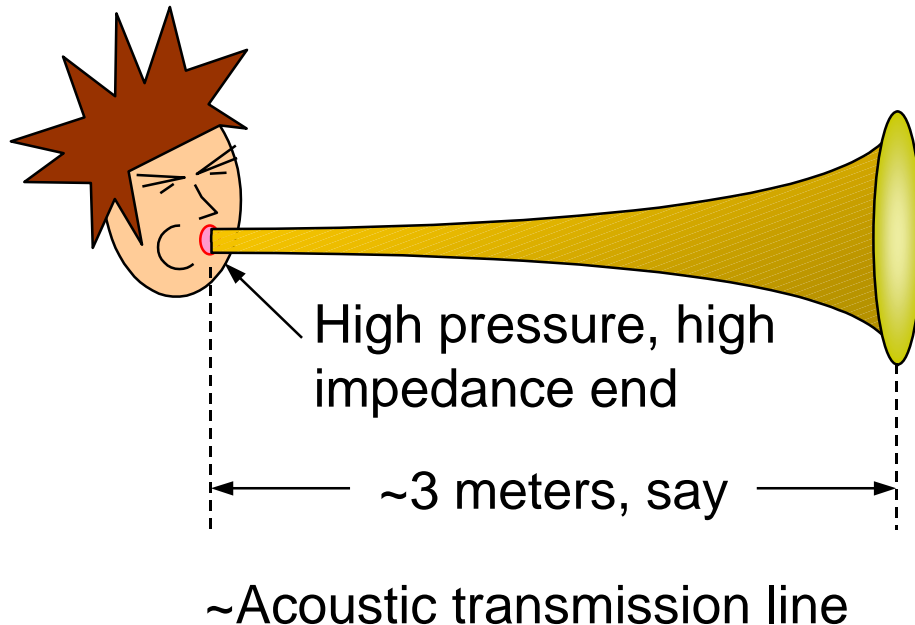

low-pressure,
low-impedance end

$$N = 8 \Rightarrow \lambda_{\max} = 4L/N$$
$$= 4 \cdot 3/8 = 1.5 \text{ meters}$$
$$f_{\min} = c_s/\lambda = \sim 300/(1.5) = 200 \text{ Hz}$$