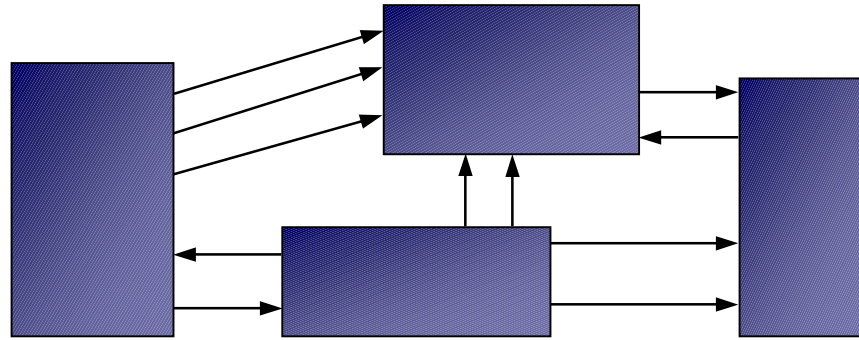


TRANSIENT SIGNALS IN COMPUTERS

Dream World:

Only 1's and 0's
Instantaneous links



Reality:


- Voltages, not 1's and 0's
- Levels and impedances matter
- Delays and transients matter
- Spurious transient waveforms generated at mismatches, can superimpose to flip bits erroneously
- RFI generated and picked up by wires can flip bits
- Ground loops matter

Paradigm:

Use Thevenin equivalent circuits for transmission lines, etc.

TEM LINE THEVENIN EQUIVALENT (1)

Basic Equations for Lossless TEM Wires:

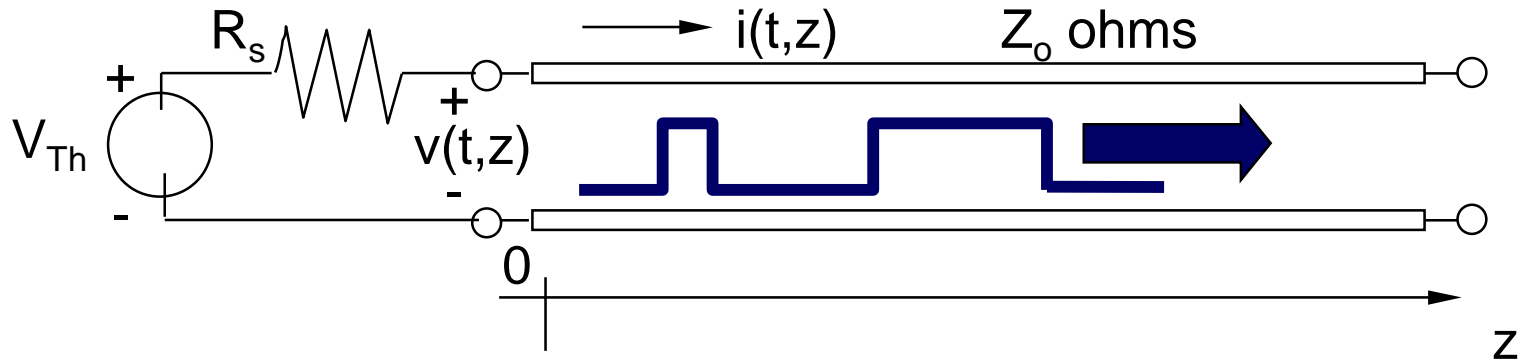

$$v(z,t) = v_+(t - z/c) + v_-(t + z/c)$$

$$i(z,t) = Y_0[v_+(t - z/c) - v_-(t + z/c)]$$

Where:

$$Y_0 = 1/Z_0 = (C/L)^{0.5}$$


**This is a “boundary value problem”
The boundary is at $z = 0$**

TEM LINE THEVENIN EQUIVALENT (2)

Boundary Value Problems, Solution Method:

- 1) Characterize waves in each medium, with unknown coefficients
- 2) Impose boundary condition equations
- 3) Solve equations for unknowns

Example: Given $V_s(t)$:

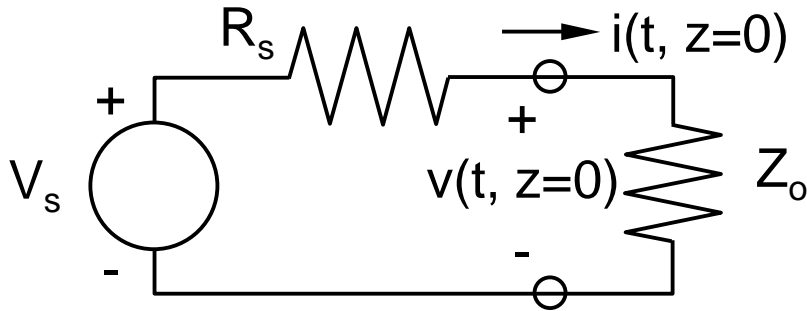


$$v(z,t) = v_+(t - z/c) + v_-(t + z/c)$$
$$i(z,t) = Y_o[v_+(t - z/c) - v_-(t + z/c)]$$

Assume $v_- = 0$ (no other sources)
Then $v(t, z = 0) = Z_o i(t, z = 0)$
Yields equivalent circuit; solve it

$$v_+(t, z=0) = (Z_o/[Z_o + R_s])V_s(t)$$
$$v_+(t, z) = (Z_o/[Z_o + R_s])V_s(t - z/c)$$


TEM LINE THEVENIN EQUIVALENT (3)

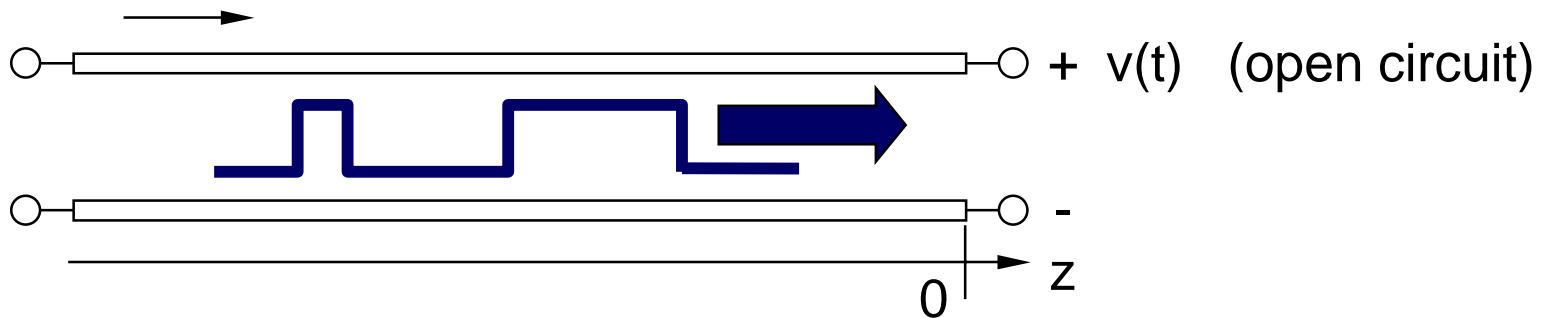Voltages at an Open Circuit: $v(z,t) = v_+(t - z/c) + v_-(t + z/c)$



Since: $i(z,t) = Y_o[v_+(t - z/c) - v_-(t + z/c)] = 0$ at $z = 0$
 Therefore: $v_+(t) = v_-(t)$ at $z = 0$, and $v(t) = 2v_+(t)$

Thevenin Equivalent for TEM Source:

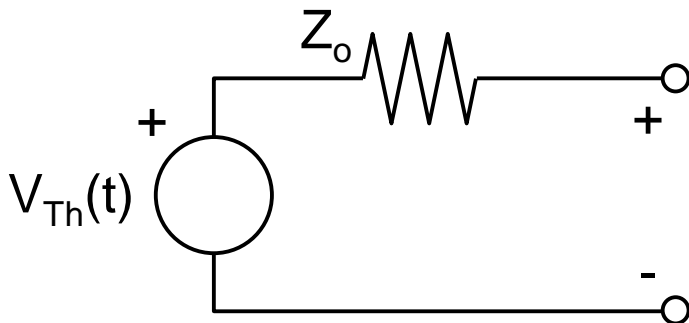


$$V_{\text{open circuit}}(t) = 2v_+(t, z = 0)$$

Therefore:

$$V_{Th}(t) = 2v_+(t, z=0)$$

TEM LINE THEVENIN EQUIVALENT (4)

Example—Resistive Load:

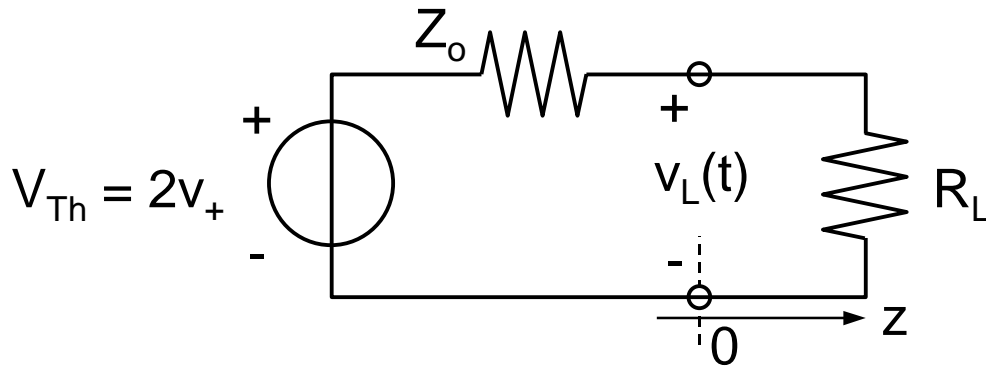

$$\begin{aligned}v_L(t) &= V_{Th} R_L / (R_L + Z_o) \\ &= v_-(t; z=0) + v_+(t; z=0)\end{aligned}$$

Therefore:



$$v_-(t; z=0) = v_L(t) - v_+(t, z=0) =$$
$$2v_+(t; z=0)[R_L / (R_L + Z_o) - 0.5] \text{ and}$$
$$\Gamma = v_- / v_+ |_{z=0} \text{ "Reflection Coefficient"}$$
$$\Gamma = 2R_L / (R_L + Z_o) - 1$$

$$\Gamma = v_- / v_+ |_{z=0} = (R_L - Z_o) / (R_L + Z_o)$$

$$\left\{ \begin{array}{l} = 1 \text{ for } R_L = \infty \\ = 0 \text{ for } R_L = Z_o \\ = -1 \text{ for } R_L = 0 \end{array} \right.$$

TEM LINE THEVENIN EQUIVALENT (5)

Example, Time-Domain Solution:

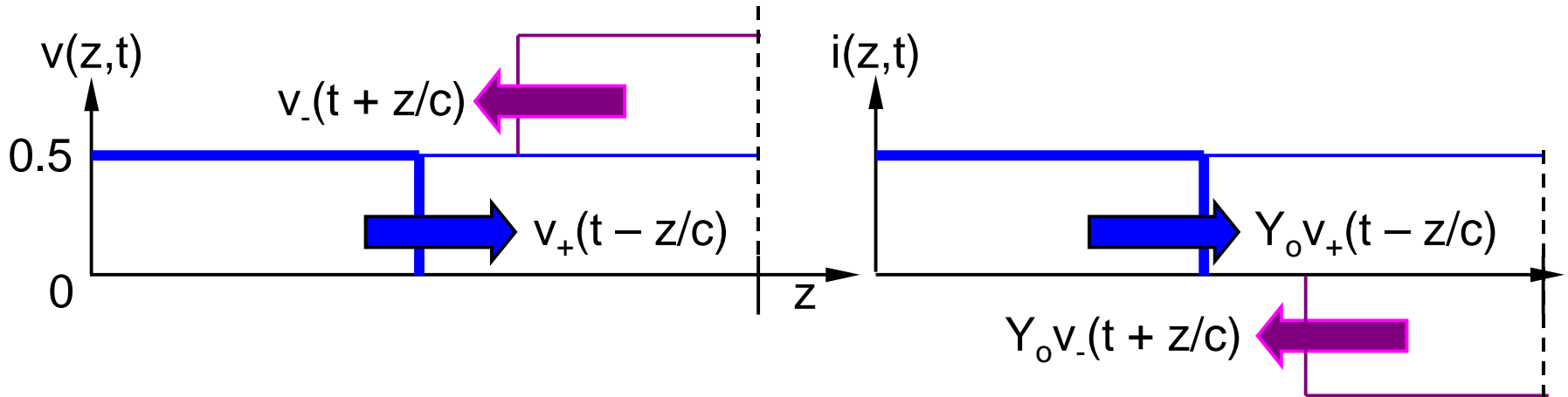
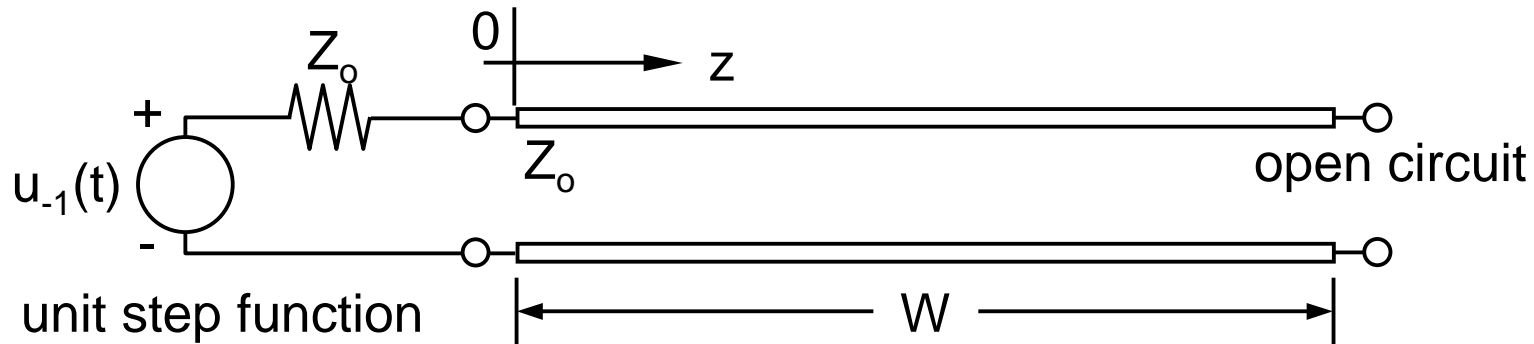


$$v(z,t) = v_+(t - z/c) + v_-(t + z/c) = 0.5[u_{-1}(t - z/c) + u_{-1}(t + z/c - 2W/c)]$$

$$i(z,t) = Y_0[v_+(t - z/c) - v_-(t + z/c)] = 0.5Y_0[u_{-1}(t - z/c) - u_{-1}(t + z/c - 2W/c)]$$

CAPACITIVELY TERMINATED TEM LINE

Example—Capacitive Load:


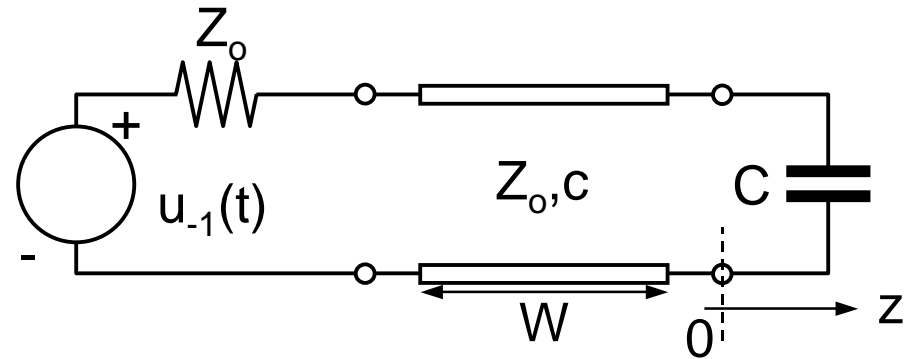
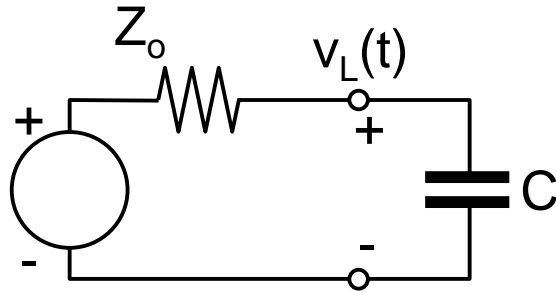


$$V_{Th} = 2v_+(t, z=0)$$

$$= 2[0.5 u_{-1}(t - W/c)]$$

$$v_L(t) = v_-(t; z=0) + v_+(t; z=0)$$

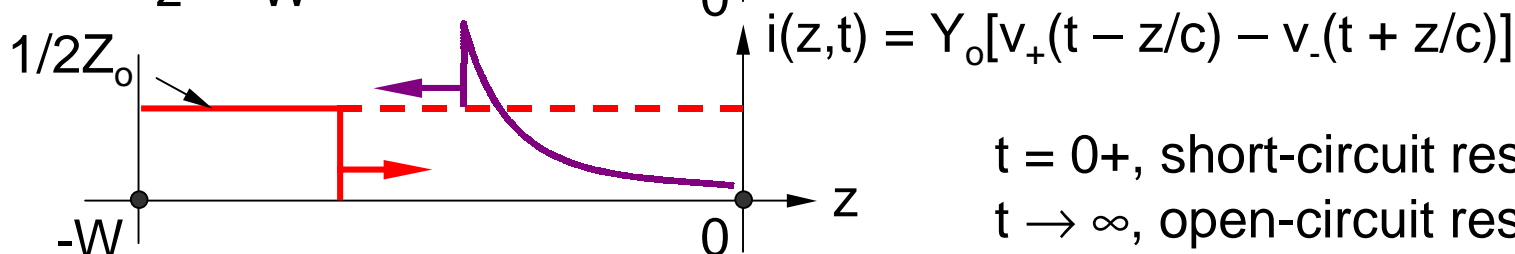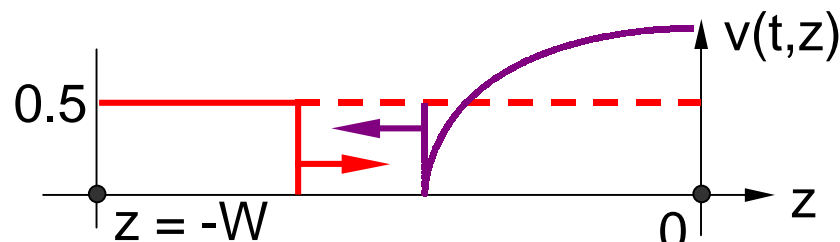
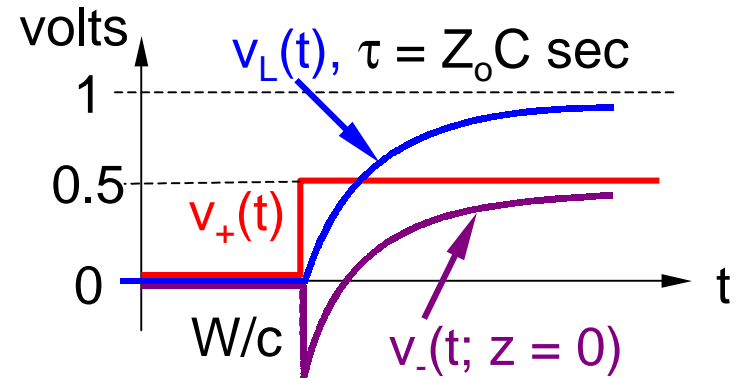
$$\text{Therefore: } v_-(t; z=0) = v_L(t) - v_+(t; z=0)$$



$t = 0+$, short-circuit response
 $t \rightarrow \infty$, open-circuit response

DIODE-TERMINATED TEM LINE

Example—Computer Circuit:

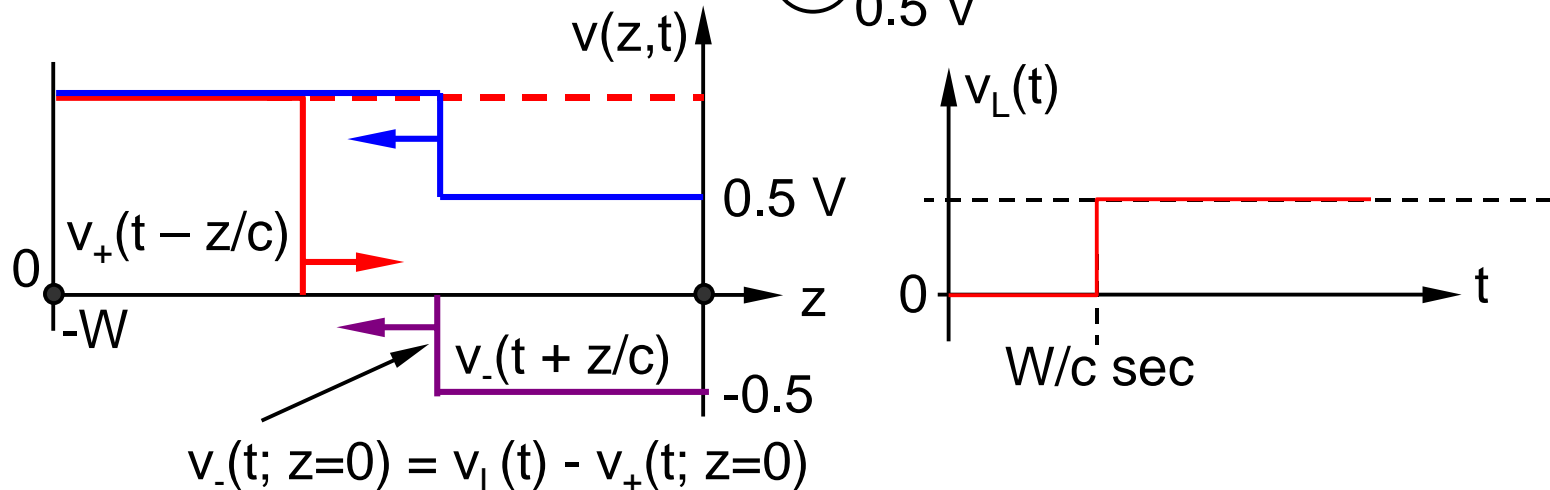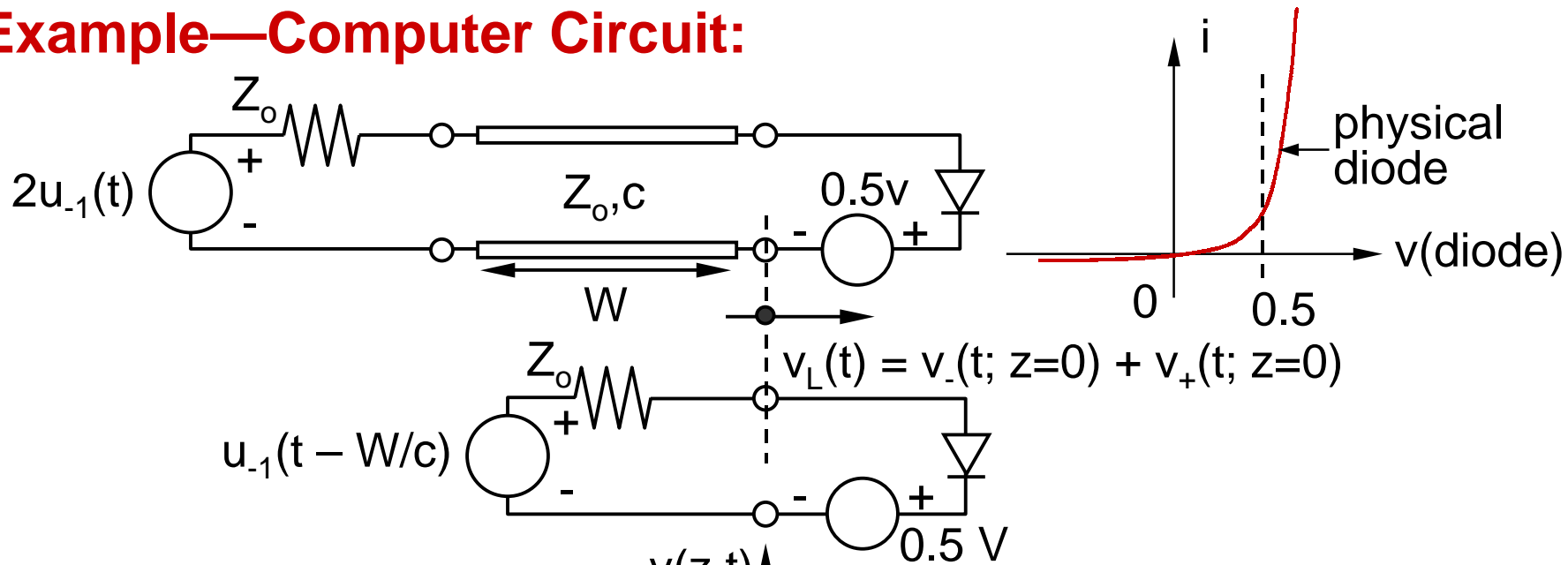

$$v(z,t) = v_+(t - z/c) + v_-(t + z/c)$$

$$i(z,t) = Y_o[v_+(t - z/c) - v_-(t + z/c)]$$



Do we violate KVL, KCL?

MISMATCHED SOURCES

Current Source:

$$\Gamma = (R_L - Z_0)/(R_L + Z_0)$$

$$= (3 - 1)/(3 + 1) = 1/2$$

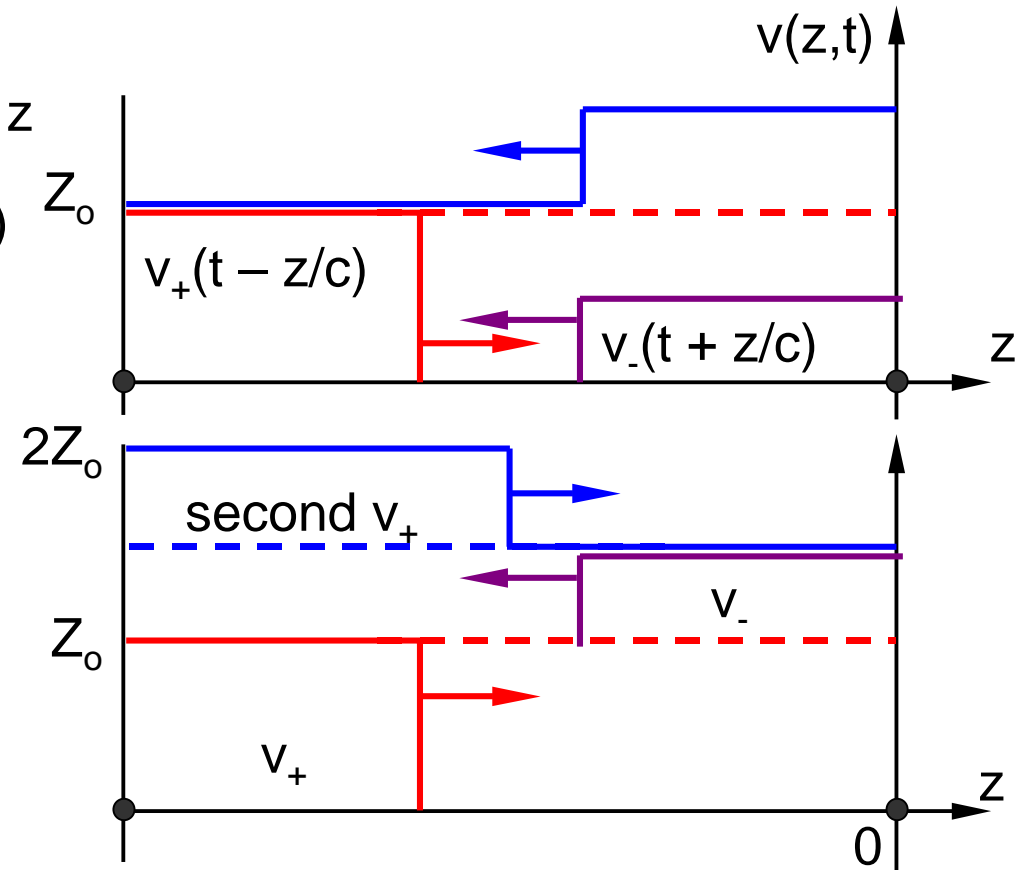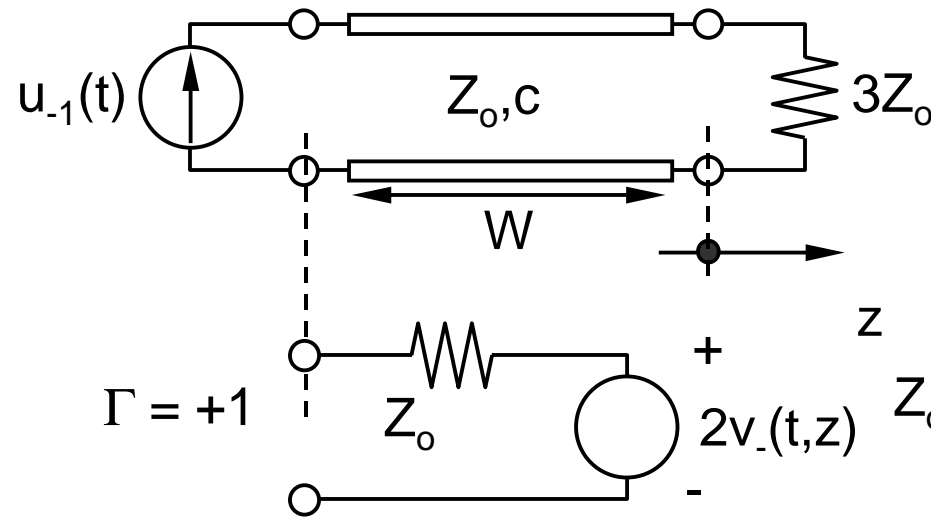

Note:
Current source and v_-
superimpose as sources